

Physics 153 Section T0H - Week 11

LR Circuits

Rik Blok

March 30, 2000

# 1 Revenge!

Bring your pencils next week so you can fill out my teaching evaluation. Finally, your chance to *grade* me! Don't worry, I won't see them until well after the term is over.

## 2 Self-inductance

When a circuit has an inductor in it, the inductor responds to changes in the current by setting up an emf

$$V_L = -L \frac{dI}{dt} \quad (1)$$

which opposes the change in current.  $L$  is the self-inductance, measured in Henries (H).

## 3 LR Circuits

The opposition to change causes the current to change exponentially over time instead of instantly,

$$I(t) - I(\infty) = [I(0) - I(\infty)] e^{-t/\tau}. \quad (2)$$

(This equation applies to any part of the circuit, not just through the inductor.)

This should look familiar. It's the exact same equation I gave you for RC circuits. The only difference is in calculating the constants.

The time constant is given by


$$\tau = L/R. \quad (3)$$

To calculate the initial and final values keep these facts in mind:

1. Initially, after a change in the circuit, the current across the inductor does not change. It stays the same as just before the change.
2. After a long time, the inductor just acts like a short-circuit.

## 4 Example

(From Tipler Ch. 26 #57.)

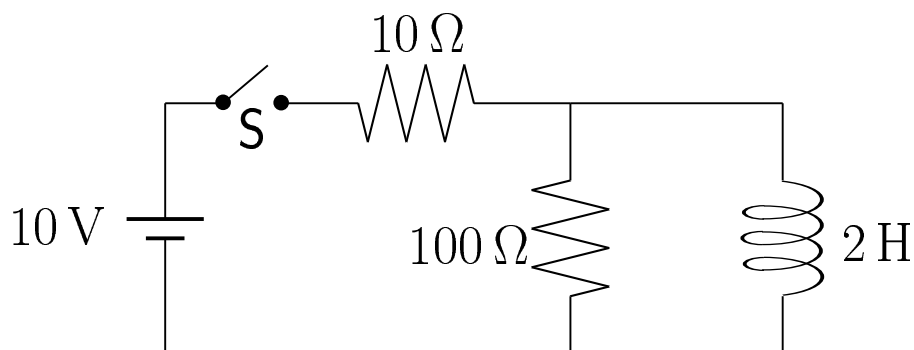


Given the circuit shown above, assume that switch  $S$  has been closed for a long time so that steady currents exist in the circuit and that the resistance of the inductor  $L$  may be considered to be zero. (a) Find the battery current, the current in the  $100\ \Omega$  resistor, and the current through the inductor. (b) Find the initial voltage across the inductor when switch  $S$  is opened. (c) Give the current in the inductor as a function of time measured from the instant of opening switch  $S$ .

# 5 Solution
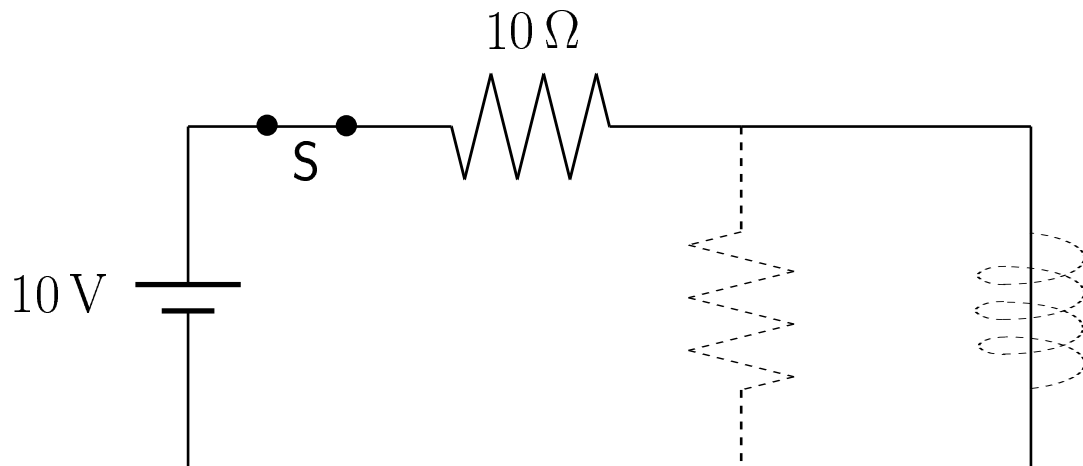
## 5.1 Part (a)

“Find the battery current, the current in the  $100\ \Omega$  resistor, and the current through the inductor.”

We’re considering the circuit a long time after the switch has been closed (let’s call this time  $t = \infty$ ) so the inductor just acts as a short-circuit across the resistor so the circuit can be drawn as:



So the circuit just consists of a battery in series with a single resistor and the currents through the battery and the inductor are

$$I_V(\infty) = I_L(\infty) = \frac{V}{R_1} = \frac{10}{10} = 1 \text{ A.} \quad (4)$$

Since the  $100\ \Omega$  resistor is short-circuited, no current passes through it,

$$I_R(\infty) = 0. \quad (5)$$

## 5.2 Part (c)

“Give the current in the inductor as a function of time measured from the instant of opening switch S.”

Note that I’m solving part (c) *before* part (b). That’s because I can use the result from part (c) to solve part (b).

When we open the switch let's reset the clock to zero ( $t = 0$ ) and denote everything after that with primes.


Recall, the general equation for the current through the inductor is

$$I'(t) - I'(\infty) = [I'(0) - I'(\infty)] e^{-t/\tau} \quad (6)$$

so we just need to fill in the constants.
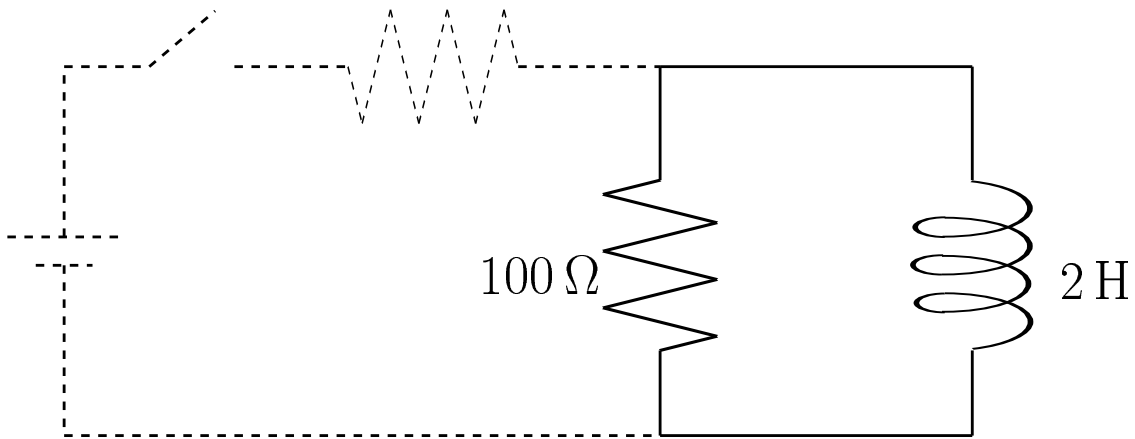
### 5.2.1 Time constant

First, let's calculate the time constant. The circuit now looks like this:



So, the time constant just depends on the inductor and the  $100\ \Omega$  resistor:

$$\tau = \frac{L}{R} = \frac{2}{100} = 0.02\ \text{s}. \quad (7)$$

### 5.2.2 Initial current

Initially, the inductor resists a change in the current so it is the same as it was just before the switch was opened,

$$I'_L(0) = I_L(\infty) = 1\ \text{A}. \quad (8)$$



### 5.2.3 Final current

After a long time the current must go to zero because there is no voltage driving it,

$$I'_L(\infty) = 0. \quad (9)$$

### 5.2.4 Current equation

Substituting all that into Eq. (6) gives

$$I'_L(t) - 0 = [(1 \text{ A}) - 0] e^{-t/(0.02 \text{ s})} \quad (10)$$

$$I'_L(t) = (1 \text{ A}) e^{-t/(0.02 \text{ s})}. \quad (11)$$

## 5.3 Part (b)

“Find the initial voltage across the inductor when switch S is opened.”

The voltage across the inductor is always given by

$$V_L = -L \frac{dI_L}{dt} \quad (12)$$

so we can just take the derivative of the current equation to get the voltage:

$$V'_L(t) = -L \frac{d}{dt} \left[ I'_L(0) e^{-t/\tau} \right] \quad (13)$$


$$= -L I'_L(0) e^{-t/\tau} \frac{-1}{\tau} \quad (14)$$

$$= \frac{L I'_L(0)}{\tau} e^{-t/\tau}. \quad (15)$$

So, at time zero,

$$V'_L(0) = \frac{L I'_L(0)}{\tau} = \frac{(2)(1)}{0.02} = 100 \text{ V}. \quad (16)$$

## 6 Assigned Problem

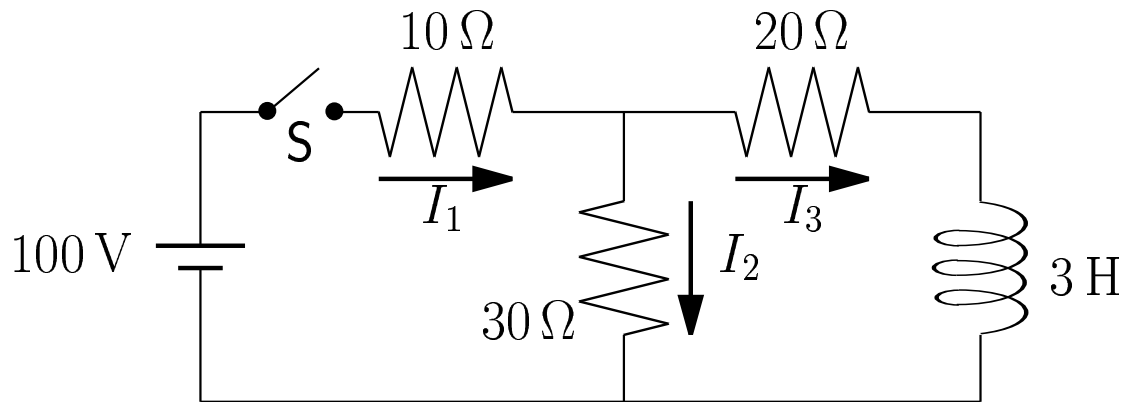

For the circuit shown above, find the currents  $I_1$ ,  $I_2$ , and  $I_3$  (a) immediately after switch S is closed and (b) a long time after switch S has been closed. After the switch has been closed for a long time, it is opened. Find the three currents (c) immediately after switch S is opened and (d) a long time after switch S was opened.