

UBC Physics 102

Lecture 8

Rik Blok



Capacitors [Text: Sect. 24-1]

- **Definition: Capacitor**
- Device that can store electric charge.
- Often constructed of two parallel plates.



- Circuit diagram symbol: $\text{--}\parallel\text{--}$
- When voltage V applied to plates they acquire charges $\pm Q$ where

$$Q = CV.$$



Outline

- △ Capacitors
- △ Capacitance
- △ Series and parallel
- △ Energy storage
- △ Dielectrics
- △ Electric current
- △ Ohm's law
- △ Resistivity
- △ End



Capacitance [Text: Sect. 24-2]

- **Definition: Capacitance, C**
- Constant of proportionality.
- Depends on details of capacitor (eg. size, shape).

● **Unit: Farad, F**

- Unit of capacitance,

$$1 F = 1 C/V.$$


● **Discussion: Capacitance**

- To derive capacitance solve for relationship between V and Q . Will find $Q \propto V$. C is proportionality constant.



Capacitance, contd

Derivation: Parallel plate capacitance

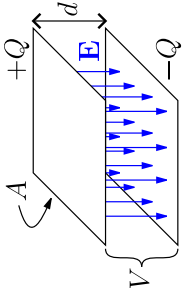

- From Gauss's law can find strength of E -field between plates,

$$E = \frac{\sigma}{\epsilon_0}$$

- σ is surface charge density, $\sigma = \frac{Q}{A}$.



Capacitance, contd

Derivation: Parallel plate capacitance, contd

- E uniform so can use $V = -E\ell$ (ignoring sign) to get

$$V = \frac{\sigma d}{\epsilon_0} = \frac{Qd}{\epsilon_0 A}$$

- Rearranging gives $Q = \frac{\epsilon_0 A}{d} V = CV$ so

$$C = \frac{\epsilon_0 A}{d}$$


- Can use similar method for other shapes.



Series and parallel [Text: Sect. 24-3]

Discussion: Review of circuit diagrams

- Lines are wires connecting components. No voltage drop.
- Battery (Symbol: $\begin{array}{c} + \\ | \\ - \end{array}$) raises voltage on + side. (Analogy: an escalator.)
- Capacitor: $\begin{array}{c} | \\ | \\ | \end{array}$
- Voltage pumps charge onto plates.
- Net voltage change over any loop must be zero. (Analogy: net height change= 0.)

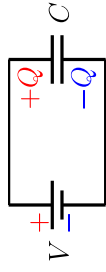


Series and parallel, contd

Definition: Parallel

- Path splits, goes across multiple components, and rejoins.
- Voltage drop identical across each path.

Derivation: Parallel capacitors

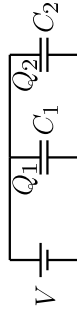

- Same voltage drop across each capacitor so $V_1 = V_2 = V$.
- Charge on capacitors: $Q_1 = C_1 V$, $Q_2 = C_2 V$.



Series and parallel, contd

• Derivation: Parallel capacitors, contd

- Total charge Q pumped onto both capacitors,
- $$Q = Q_1 + Q_2 = C_1V + C_2V$$
$$= (C_1 + C_2)V.$$
- Equivalent to a single capacitor, $Q = C_{eq}V$, where

$$C_{eq} = C_1 + C_2.$$


• Definition: Series

- Components are connected end to end.
- Total voltage drop is sum of all components.



Series and parallel, contd

• Derivation: Series capacitors

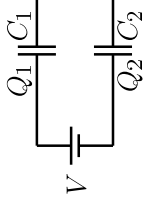

- Charge conserved so + charge built up on capacitor 1 must leave – charge on capacitor 2, and vice versa.
- So charge the same on both capacitors, $Q_1 = Q_2 = Q$.
- Voltage drop across capacitors: $V_1 = \frac{Q}{C_1}$, $V_2 = \frac{Q}{C_2}$.



Series and parallel, contd

• Derivation: Series capacitors, contd

- Total voltage drop across capacitors equal to voltage climb across battery,

$$V = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2}$$
$$= \left(\frac{1}{C_1} + \frac{1}{C_2} \right) Q.$$

- Equivalent to a single capacitor, $V = \frac{1}{C_{eq}}Q$, where

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}.$$



Series and parallel, contd

• Discussion: Series and parallel capacitors

- Can use these “replacement” rules to simplify complex configurations of capacitors.
- Rarely not able to divide circuit into series and parallel. But voltage rules (eg. = 0 over loop), charge conservation, and other laws still apply.

• Interactive Quiz: PRS 08a



Energy storage [Text: Sect. 24-4]

- **Discussion: Energy storage**
 - Have to do work to charge capacitor.
 - Work stored as potential energy in capacitor.
 - Energy stored in electric field (between plates).
- **Derivation: Potential energy**
 - Can derive how much energy stored in capacitor.
 - Consider situation where voltage \hat{V} ramped up gradually from $\hat{V} = 0$ to $\hat{V} = V$.
 - Charge on plates when ramp voltage is \hat{V} is $Q = C\hat{V}$.
 - Recall, energy of charge Q at voltage \hat{V} is $U = Q\hat{V}$.
 - But both Q and \hat{V} changing so can't use $U = QV$.



Energy storage, contd

- **Derivation: Potential energy, contd**
 - But if voltage change small enough ($d\hat{V} \rightarrow 0$) then can assume Q constant over change.
 - Increase in potential energy is
$$dU = Q d\hat{V} = C\hat{V} d\hat{V}.$$
 - Total potential is sum of increments, $U = \int_0^V C\hat{V} d\hat{V}$,

$$U = \frac{1}{2}CV^2 = \frac{1}{2} \frac{Q^2}{C}.$$

- Last expression comes from $Q = CV$.



Dielectrics [Text: Sect. 24-5]

- **Definition: Dielectric constant, K**
 - Amount by which material between plates increases capacitance,

$$C = KC_0.$$

- C_0 is capacitance in vacuum (or air, roughly).
- $K > 1$ for dielectric.
- Dielectric works by polarizing, setting up electric field contrary to original.
- Changing C changes potential energy U capacitor will hold.



Dielectrics, contd

- **Interactive Quiz: PRS 08b**
- **Example: Pr. 75**
 - A parallel-plate capacitor is isolated with a charge $\pm Q$ on each plate. If the separation of the plates is halved and a dielectric (constant K) is inserted in place of air, by what factor does the energy storage change? To what do you attribute the change in stored potential energy?
- **Solution: Pr. 75**
 - We know charge Q held constant.



Dielectrics, contd

• Solution: Pr. 75, contd

- So $U = \frac{1}{2} \frac{Q^2}{C}$ gives potential energy. Initially,

$$U_0 = \frac{1}{2} \frac{Q^2}{C_0}$$


- Let's think about this in 2 steps:
- Step 1: halving the separation.
- From $C = \frac{\epsilon_0 A}{d}$ this has the effect of doubling the capacitance,

$$C_1 = 2C_0.$$



Dielectrics, contd

• Solution: Pr. 75, contd

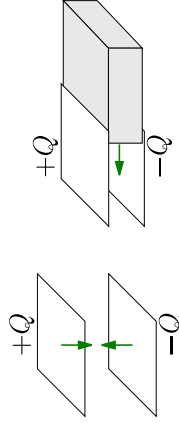

- Step 1: Releasing plates allowed them to move closer together (attraction of plates).
- Step 2: Capacitor drew in dielectric when we brought it close (dielectric polarized in proximity of capacitor then attracted to it).



Dielectrics, contd

• Solution: Pr. 75, contd

- Step 2: inserting the dielectric.
- From $C = KC_0$ the capacitance is increased by a factor K ,

$$C_2 = KC_1 = 2KC_0.$$

- Now the potential energy is

$$U_2 = \frac{1}{2} \frac{Q^2}{C_2} = \frac{1}{2K} U_0.$$

- So potential energy decreases by ratio of $2K$.
- In each step, the potential energy decreased.
- So both changes happened spontaneously.



Electric current [Text: Sect. 25-2]

• Definition: Electric current, I

- Rate of charge flow past a point,

$$I = \frac{dQ}{dt}.$$

- Current flows if voltage different between points.
- Analogy: voltage \leftrightarrow height, current \leftrightarrow river current.

• Unit: Ampere, A


- Unit of current

$$1 A = 1 C/s.$$



Electric current, contd

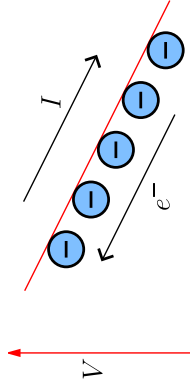- **Discussion: Convention**
- Current said to flow from high potential to low (historical).
- Actually, electrons flowing from low to high.
- Doesn't matter, except in rare cases.



UBC Physics 102: Lecture 8, July 11, 2008 - p. 21/25

<https://www.zoology.ubc.ca/~f1kblak/phys102/Lecture/>

Ohm's law [Text: Sect. 25-3]

- **Definition: Ohm's law**
 - Current I proportional to voltage difference V that caused it, $V \propto I$, or
- $$V = IR.$$
- R is proportionality constant, called **resistance**.
 - Water analogy: $\frac{1}{R} \leftrightarrow$ cross-section of pipe (restricts flow).
 - Ohm's law states R is constant.
 - Not always true (will see in lab).



UBC Physics 102: Lecture 8, July 11, 2008 - p. 22/25

<https://www.zoology.ubc.ca/~f1kblak/phys102/Lecture/>

Ohm's law

- **Unit: Ohm, Ω**
- Units of resistance,
 $1 \Omega = 1 \text{ V/A}.$
- **Definition: Resistor**
- A circuit component that obeys Ohm's law.
- Has a specific resistance, R .
- Circuit diagram symbol: zigzag
- R depends on material, size, shape, etc.




UBC Physics 102: Lecture 8, July 11, 2008 - p. 22/25

<https://www.zoology.ubc.ca/~f1kblak/phys102/Lecture/>

Resistivity [Text: Sect. 25-4]

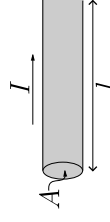- **Definition: Resistivity, ρ**
- Empirically found that metals obey



$$R = \rho \frac{l}{A}.$$

- Proportionality constant, ρ , depends on material and temperature, not much else.

Interactive Quiz: PRS 08c



UBC Physics 102: Lecture 8, July 11, 2008 - p. 24/25

<https://www.zoology.ubc.ca/~f1kblak/phys102/Lecture/>

End

● Practice Problems:

- Ch. 24: Q. 3, 7, 9, 13, 17.
- Ch. 24: Pr. 1, 3, 5, 7, 9, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 39, 41, 43, 45, 47, 51, 53, 55, 57, 59, 67, 69, 71, 73, 75, 77, 81, 83, 85, 87.

● Midterm Test: #2

- Second 60 min. test on Mon (Jul 14).
- Will cover all material in Lectures 4–8 (except Ch. 25).

● Interactive Quiz: Feedback

● Tutorial Question: tut08

