

UBC Physics 102

Lecture 9

Rik Blok



Outline

- ▷ Electric power
- ▷ Alternating current
- ▷ End



Electric power [Text: Sect. 25-5]

- **Definition: Power**
- Rate energy is delivered to component,

$$P = \frac{dU}{dt}.$$

- Energy usually turned into heat.
- Energy delivered by charges moving through potential difference.
- Across potential V energy of little charge dq changes by $dU = dqV$ so power consumed is

$$P = \frac{dq}{dt}V = IV.$$



Electric power, contd

- **Unit: Watt, W**
- Unit of power,

$$1 \text{ W} = 1 \text{ J/s.}$$

- **Discussion: Power in resistor**
- Across resistance R voltage drop is $V = IR$.
- So power delivered is

$$P = IV = I^2R = \frac{V^2}{R}.$$

- Only true for constant R .



Alternating current [Text: Sect. 25-7]

- **Interactive Quiz: PRS 09a**
- **Definition: Alternating current, ac**

- ac generated by oscillating voltage,

$$V = V_0 \sin \omega t.$$

- V_0 is **peak voltage**, magnitude of V .
- Current across resistor R is


$$I = \frac{V}{R} = I_0 \sin \omega t.$$

- $I_0 = \frac{V_0}{R}$ is **peak current**, magnitude of I .



Alternating current, contd

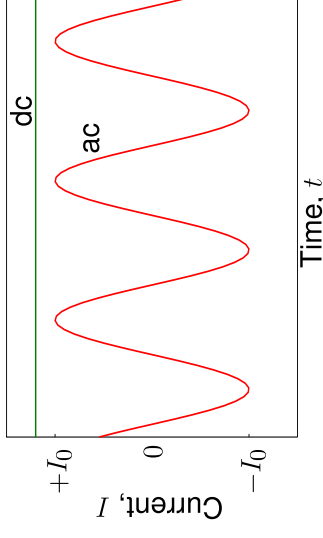- **Definition: Alternating current, ac, contd**
- So current alternates in direction.



Alternating current, contd

- **Derivation: RMS voltage and current, V_{RMS} and I_{RMS}**

- Consider sinusoidal quantity

$$y = y_0 \sin \omega t$$

- Average is zero but can compute an “effective” average, called RMS.
- RMS = Root (of the) Mean (of the) Square.
- 3 Steps. Step 1: Square.


$$y_S = y^2 = y_0^2 \sin^2 \omega t.$$



Alternating current, contd

- **Derivation: RMS voltage and current, V_{RMS} and I_{RMS} , contd**

- Step 2: Mean (average).

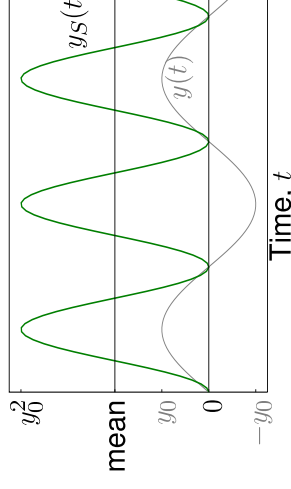

$$y_{MS} = \text{mean}(y_S) = \frac{1}{2} y_0^2.$$



Alternating current, contd

- **Derivation: RMS voltage and current, V_{RMS} and I_{RMS} , contd**

- Step 3: Root.

$$y_{RMS} = \sqrt{y_{MS}} = \frac{1}{\sqrt{2}}y_0.$$

- Applies to sinusoidal voltage and current,

$$V_{RMS} = \frac{1}{\sqrt{2}}V_0, \quad I_{RMS} = \frac{1}{\sqrt{2}}I_0.$$

- RMS values more useful than peak values.
- Most ac voltages and currents reported are RMS.

<https://www.zoo.ubc.ca/~f1bb10k/phys102/lecture/>

UBC Physics 102: Lecture 9, July 14, 2009–p. 9/12



Alternating current, contd

- **Discussion: Average power, \bar{P} , contd**

- More useful to know average power, \bar{P} . Average of $\sin^2 \omega t$ is $\frac{1}{2}$ so

$$\bar{P} = \frac{1}{2}I_0V_0.$$

- Or, written in terms of I_{RMS} and V_{RMS} ,

$$\bar{P} = I_{RMS}V_{RMS}.$$

- This is ac equivalent of power for dc circuit, $P = IV$.



<https://www.zoo.ubc.ca/~f1bb10k/phys102/lecture/>

UBC Physics 102: Lecture 9, July 14, 2009–p. 11/12

Alternating current, contd

- **Derivation: RMS voltage and current, V_{RMS} and I_{RMS} , contd**

- Example: RMS wall voltage is 120 V, peak is $V_0 = \sqrt{2}V_{RMS} = 170$ V.

- **Interactive Quiz: PRS 09b**

- **Discussion: Average power, \bar{P}**

- If V and I not constant then nor is power.
- If sinusoidal then power at any moment is

$$P = IV = I_0V_0 \sin^2 \omega t.$$

<https://www.zoo.ubc.ca/~f1bb10k/phys102/lecture/>

UBC Physics 102: Lecture 9, July 14, 2009–p. 10/12



End

- **Practice Problems:**

- Ch. 25: Q. 1, 3, 5, 7, 11, 17.
- Ch. 25: Pr. 1, 3, 5, 7, 9, 11, 13, 15, 25, 27, 29, 31, 33, 35, 37, 39, 43, 45, 47, 49, 55, 57, 59, 65, 67, 69, 71, 75.

- **Interactive Quiz: Feedback**



<https://www.zoo.ubc.ca/~f1bb10k/phys102/lecture/>

UBC Physics 102: Lecture 9, July 14, 2009–p. 12/12