

UBC Physics 102

Lecture 10

Rik Blok




Outline

- △ Emf
- △ Resistors in series and parallel
- △ Kirchoff's rules
- △ RC Circuits
- △ End



Emf [Text: Sect. 26-1]

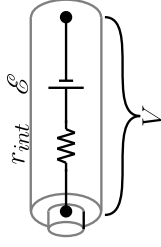- **Definition: Emf, \mathcal{E}**
 - Theoretical maximum voltage gain of battery.
 - Historically called *electromotive force* but is actually a voltage not a force.
- **Discussion: Batteries**
 - Batteries have internal resistance, r_{int} .
 - Some voltage loss across r_{int} .




Emf, contd

- **Discussion: Batteries, contd**
 - When current I flowing net voltage across terminals is
$$V = \mathcal{E} - r_{int}I.$$
 - \mathcal{E} and r_{int} properties of battery (Lab 3).
 - In problems you may see \mathcal{E} instead of V . Assume no internal resistance.



Resistors in series and parallel [Text: Sect. 26-2]

Derivation: Resistors in series

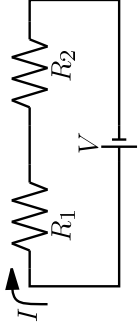

- No branches so same current goes through both resistors.
- Voltage drop across each resistor: $V_1 = IR_1$, $V_2 = IR_2$.
- Voltage drop must equal voltage gain of battery,

$$\begin{aligned} V &= V_1 + V_2 \\ &= I(R_1 + R_2). \end{aligned}$$




<https://www.zoo.ubc.ca/~f1kblak/phys102/lecture/>

UBC Physics 102: Lecture 10, July 15, 2020—p. 523

Resistors in series and parallel, contd

Derivation: Resistors in parallel

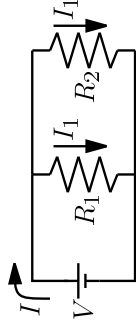

- Voltage drop must be same across both paths so, $I_1 = \frac{V}{R_1}$, $I_2 = \frac{V}{R_2}$.
- Current splits across branch,

$$\begin{aligned} I &= I_1 + I_2 \\ &= V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_{eq}}. \end{aligned}$$



<https://www.zoo.ubc.ca/~f1kblak/phys102/lecture/>

UBC Physics 102: Lecture 10, July 15, 2020—p. 723

Resistors in series and parallel, contd

Derivation: Resistors in series, contd

- From Ohm's law $V = IR$ resistors in series equivalent to one resistor with resistance

$$R_{eq} = R_1 + R_2 + \dots$$



<https://www.zoo.ubc.ca/~f1kblak/phys102/lecture/>

UBC Physics 102: Lecture 10, July 15, 2020—p. 623

Resistors in series and parallel, contd

Derivation: Resistors in parallel, contd

- Resistors in parallel equivalent to one resistor with resistance R_{eq} , where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}.$$

- Can simplify (most) complex circuits by replacing series and parallel combinations by equivalents.

Interactive Quiz: PRS 10a




<https://www.zoo.ubc.ca/~f1kblak/phys102/lecture/>

UBC Physics 102: Lecture 10, July 15, 2020—p. 823

Resistors in series and parallel, contd

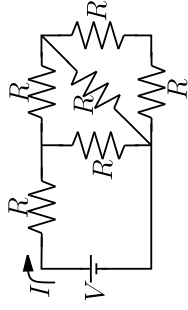• Example: Pr. 11

- What is the net resistance of the circuit connected to the battery as shown?



• Solution: Pr. 11


- To simplify the circuit we need to find a set of resistors in series or parallel.




Resistors in series and parallel, contd

• Solution: Pr. 11, contd

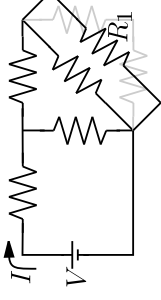- 2 in series at the bottom right, the equivalent resistance is $R_1 = 2R$.



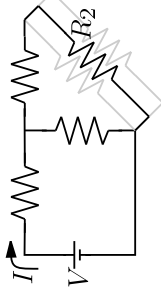
- Parallel: $\frac{1}{R_2} = \frac{1}{R} + \frac{1}{2R}$, or $R_2 = \frac{2}{3}R$.




Resistors in series and parallel, contd

• Solution: Pr. 11, contd

- Series: $R_3 = \frac{5}{3}R$.

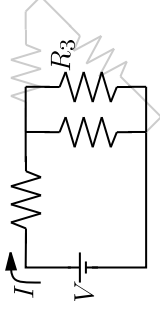

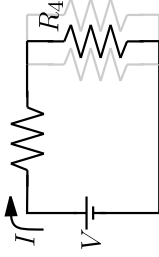
- Parallel: $\frac{1}{R_4} = \frac{1}{R} + \frac{3}{5R}$, or $R_4 = \frac{5}{8}R$.



Resistors in series and parallel, contd

• Solution: Pr. 11, contd

- Series: $R_5 = \frac{13}{8}R$.

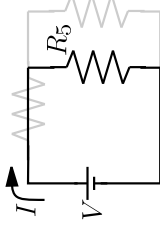


- So the net resistance is $R_5 = \frac{13}{8}R$.



Kirchhoff's rules [Text: Sect. 26-3]

Discussion: Kirchhoff's rules

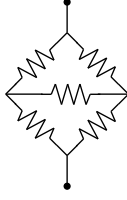- Can't simplify every combination. For example:




- Can't isolate any parallel or series combinations.
- Have to go back to basics.



Kirchhoff's rules, contd

Definition: Kirchhoff's branch rule

- At a branch

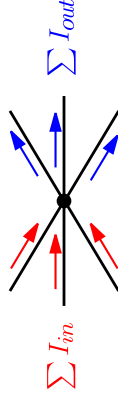

$$\sum I_{in} = \sum I_{out}.$$

- Follows from conservation of charge.


- Hint: sometimes you don't know the direction of the current. Then just guess and work out the answer. If $I < 0$ then you know it's going the other direction.



Kirchhoff's rules, contd

Definition: Kirchhoff's loop rule

- Around a loop

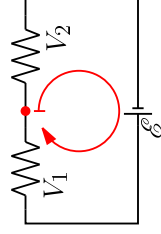

$$\sum V = 0.$$

- Follows from conservation of energy.

Interactive Quiz: PRS 10b



Discussion: Combinations of batteries

- Batteries can be arranged in series, parallel, or even opposition (head to head).
- Rule: voltage gain if battery inline with current (current goes from - battery terminal to +). Voltage drop if battery reversed (opposes current).
- Kirchhoff's rules apply.

Interactive Quiz: PRS 10c



RC Circuits [Text: Sect. 26-4]

Discussion: RC Circuits


- Circuits can contain both resistors and capacitors.
- Resistors limit current so it takes time for charge to build up on capacitor.
- In steady state no current through capacitor.
- Current decays exponentially over time,

$$I(t) = I_0 e^{-t/\tau}.$$



RC Circuits, contd

Discussion: RC Circuits, contd

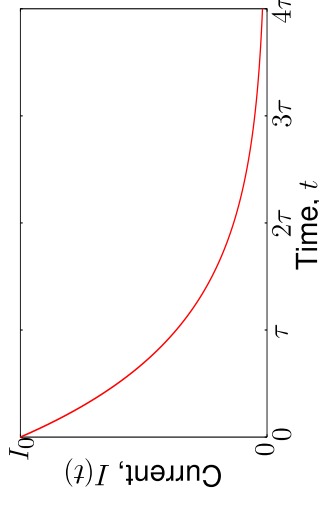

- τ is time it takes for current to drop close (about $\frac{2}{3}$ of the way) to zero.



RC Circuits, contd

Discussion: RC Circuits, contd

- Current is rate of change of charge on capacitor so charge (and voltage, $V = \frac{Q}{C}$) approach final value exponentially,

$$\begin{aligned} Q(t) - Q_\infty &= (Q_0 - Q_\infty)e^{-t/\tau}, \\ V(t) - V_\infty &= (V_0 - V_\infty)e^{-t/\tau}. \end{aligned}$$

- Use what you know about initial conditions and steady states to find I_0 , Q_0 , V_0 , Q_∞ , and V_∞ .



RC Circuits, contd

Definition: Time constant, τ

- In simple circuits, with just one capacitor and one resistor in series,

$$\tau = RC.$$

- Doesn't hold if more capacitors or resistors. But may be able to simplify using series/parallel rules.


Example: Charging a capacitor

- In a circuit with a battery \mathcal{E} , resistor R , and capacitor C (initially uncharged) in series, what is the current I as a function of time?



RC Circuits, contd

• Solution: Charging a capacitor

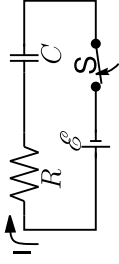

- In this simple circuit the time constant is $\tau = RC$.
- We know $I(t) = I_0 e^{-t/\tau}$ so we need to find I_0 .
- I_0 is the current at the instant the capacitor starts charging (when the switch S is closed).
- Initially the capacitor is uncharged, $Q_0 = 0$. So $V_0 = \frac{Q_0}{C} = 0$.



End

• Practice Problems:

- Ch. 26: Q. 3, 7, 9, 11, 13, 15, 17, 19.
- Ch. 26: Pr. 1, 3, 5, 7, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 33, 35, 37, 41, 43, 45, 63, 65, 67, 69, 71, 73, 75, 77, 79, 81, 83.

• Interactive Quiz: Feedback

• Tutorial Question: tut10



RC Circuits, contd

• Solution: Charging a capacitor, contd

- Then the only voltage drop in the circuit is the resistor, $V = I_0 R$, and from Kirchoff's loop rule,

$$\mathcal{E} = I_0 R.$$

- So $I_0 = \frac{\mathcal{E}}{R}$ and the current as a function of time is

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/(RC)}. \quad \square$$

• Interactive Quiz: PRS 10d

