

# UBC Physics 102


## Lecture 14

Rik Blok



## LR circuits [Text: Sect. 30-4]

### Discussion: LR circuits

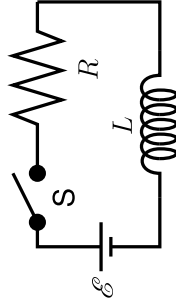

- When switch S closed, current gradually increases from zero.
- When current still small, little voltage lost in resistor,  $V_R = IR \approx 0$ .
- So most voltage lost in inductor,  $V_L \approx \mathcal{E}$  (Kirchhoff's loop rule).



## Outline

- ▷ LR circuits
- ▷ LRC circuits
- ▷ End



## LR circuits, contd

### Discussion: LR circuits, contd

- So  $V_L$  starts at maximum and falls off to zero.
- Eventually  $V_L \rightarrow V_\infty = 0$  and inductor just acts like regular wire (can be ignored).
- Current changes from initial  $I_0$  to final  $I_\infty$  exponentially,

$$\begin{aligned} V_L - V_\infty &= (V_0 - V_\infty)e^{-t/\tau}, \\ I - I_\infty &= (I_0 - I_\infty)e^{-t/\tau}. \end{aligned}$$

- In this case  $I_0 = 0$  but not always.



## LR circuits, contd

### Discussion: LR circuits, contd

- Time constant (time to get  $\sim 2/3$  of the way) is

$$\tau = \frac{L}{R}$$

- Time constant only applies to simple circuit with one  $L$  and  $R$  in series.
- So can determine behaviour by just finding values of  $V_0$ ,  $I_0$ , and  $I_{\infty}$ .
- Similar to RC circuits.

### Interactive Quiz: PRS 14a



<https://www.zoo.ubc.ca/~f1kblak/phys102/Lecture/>

UBC Physics 102: Lecture 14, July 21, 2020—p. 5/13

## LR circuits, contd

### Example: Pr. 54

- Two tightly wound solenoids have the same length and circular cross-sectional area. But solenoid 1 uses wire that is half as thick as solenoid 2. (a) What is the ratio of their inductances? (b) What is the ratio of their inductive time constants?

### Solution: Pr. 54

- (a) What is the ratio of their inductances?
  - If the wire 2 is twice as thick then it can only fit half as many turns of the wire over the same length so  $N_1 = 2N_2$ .



<https://www.zoo.ubc.ca/~f1kblak/phys102/Lecture/>

UBC Physics 102: Lecture 14, July 21, 2020—p. 6/13

## LR circuits, contd

### Solution: Pr. 54, contd

- The inductance of a solenoid is  $L = \frac{\mu_0 N^2 A}{l}$  and both are the same in every respect expect  $N$  so

$$\frac{L_1}{L_2} = \frac{N_1^2}{N_2^2} = \frac{2^2}{1^2} = 4.$$

- (b) What is the ratio of their inductive time constants?

- The resistance of the wire in a solenoid is  $R = \rho \frac{l_w}{A_w}$  where  $l_w$  is now the total length of wire and  $A_w$  is the cross-sectional area of the wire itself.

- Again, because we can only fit half as many turns on coil 2,  $l_{w1} = 2l_{w2}$ .



<https://www.zoo.ubc.ca/~f1kblak/phys102/Lecture/>

UBC Physics 102: Lecture 14, July 21, 2020—p. 7/13

## LR circuits, contd

### Solution: Pr. 54, contd

- If wire 2 is twice as thick then it has  $A_{w2} = 4A_{w1}$  the cross-sectional area.

- So the ratio of the wires' resistances is

$$\frac{R_1}{R_2} = \left( \frac{l_{w1}}{l_{w2}} \right) \left( \frac{A_{w2}}{A_{w1}} \right) = (2)(4) = 8.$$

- Finally, the time constant is  $\tau = L/R$  so

$$\frac{\tau_1}{\tau_2} = \left( \frac{L_1}{L_2} \right) \left( \frac{R_2}{R_1} \right) = (4) \left( \frac{1}{8} \right) = \frac{1}{2}. \quad \square$$




<https://www.zoo.ubc.ca/~f1kblak/phys102/Lecture/>

UBC Physics 102: Lecture 14, July 21, 2020—p. 8/13

## LRC circuits [Text: Sect. 30-5,6]

### Derivation: LC circuits

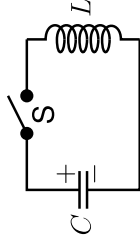


- Can construct circuit with just inductor and capacitor.
- What happens if  $C$  initially charged when  $S$  closed?
- Kirchoff's loop rule:

$$V_C + V_L = 0 = \frac{Q}{C} - L \frac{dI}{dt}.$$


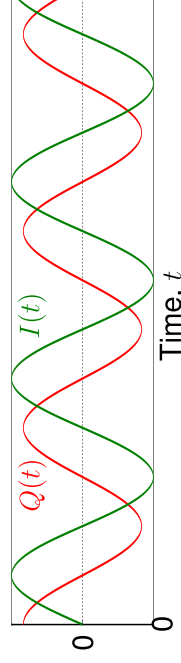
## LRC circuits, contd

- **Derivation: LC circuits, contd**
- Charge and current both oscillate.
- Frequency  $\omega_0$  determined by  $L$  and  $C$ .
- $I = -\frac{dQ}{dt}$  so current lags charge.



- Stored energy oscillates between capacitor and inductor.

### Interactive Quiz: PRS 14b



## LRC circuits, contd

### Derivation: LC circuits, contd

- Charge lost off capacitor  $-\frac{dQ}{dt}$  generates current  $I$ ,
- $$I = -\frac{dQ}{dt}.$$

- So charge related to its own second derivative,

$$\frac{Q}{C} = -L \frac{d^2Q}{dt^2}.$$


- Solution is oscillation,  $Q(t) = Q_0 \cos(\omega_0 t)$  where

$$\omega_0 = \frac{1}{\sqrt{LC}}.$$


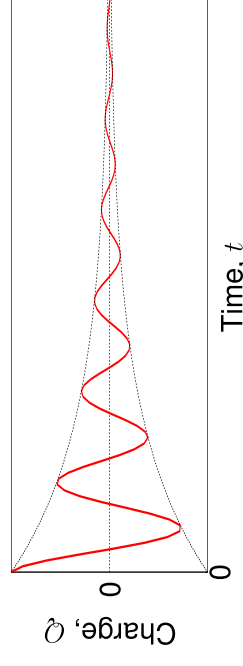
## LRC circuits, contd

- **Discussion: LRC circuits**
- If circuit contains resistance then power lost in each cycle.
- So amplitude decreases (damped oscillations).



- Can supply oscillating power to compensate for loss.



## End

### ● Practice Problems:

- Ch. 30: Q. 9, 11, 13, 15, 17, 19.
- Ch. 30: Pr. 7, 13, 15, 17, 25, 27, 29, 31, 33, 35, 45.

### ● Interactive Quiz: Feedback



<https://www.zoology.ubc.ca/~trikbak/phys102/lecture/>

UBC Phys 102 Lecture 14, July 21, 2018 - p. 13/13