

# UBC Physics 102

## Lecture 15

Rik Blok



## Outline

- ▷ AC source
- ▷ R circuits
- ▷ L circuits
- ▷ C circuits
- ▷ LRC circuits
- ▷ Resonance
- ▷ End




## AC source [Text: Sect. 31-1]

- **Definition: AC source**
  - Generates an alternating (sinusoidal unless otherwise stated) current,

$$I = I_0 \sin \omega t.$$

- Angular frequency  $\omega$  related to frequency  $f$  and period  $T$  by

$$\omega = 2\pi f = \frac{2\pi}{T}.$$

- Circuit symbol: 

- Note: multimeters read RMS values, not peak.



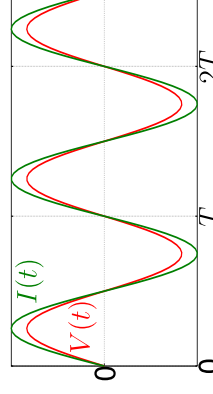
## R circuits [Text: Sect. 31-2]

- **Discussion: R circuits**



- Voltage drop across resistor,  $V = IR = I_0 R \sin \omega t$  so voltage amplitude is  $V_0 = I_0 R$ .



## L circuits [Text: Sect. 31-3]

- **Discussion: R circuits, contd**

- RMS voltage,  $V_{\text{RMS}} = I_{\text{RMS}}R$ .

- **Interactive Quiz: PRS 15a**

- **Discussion: L circuits**



- By Kirchoff's loop rule,

$$\begin{aligned} V &= L \frac{dI}{dt} = L \frac{d}{dt} I_0 \sin \omega t \\ &= \omega L I_0 \cos \omega t. \end{aligned}$$



## L circuits, contd

- **Definition: Inductive reactance,  $X_L$**
- Voltage amplitude is  $V_0 = \omega L I_0$ .
- Multimeter will give readings  $V_{\text{RMS}} = I_{\text{RMS}} X_L$  where

$$X_L = \omega L.$$



- $X_L$  called *inductive reactance*.
- Like resistance except current out of phase with voltage.



## L circuits, contd

- **Discussion: L circuits, contd**

- Current lags voltage by  $90^\circ$ .

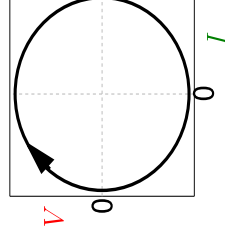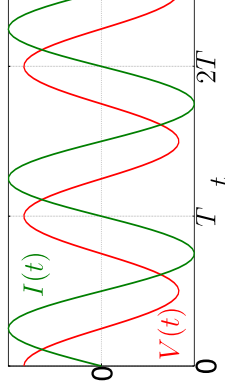

## C circuits [Text: Sect. 31-4]

- **Discussion: C circuits**



- By Kirchoff's loop rule,  $V = Q/C$ .
- How does this relate to current?  $I = \frac{dQ}{dt}$  so

$$\frac{dV}{dt} = \frac{I}{C} = \frac{I_0}{C} \sin \omega t.$$


- **Solution is**

$$V = -\frac{I_0}{\omega C} \cos \omega t.$$


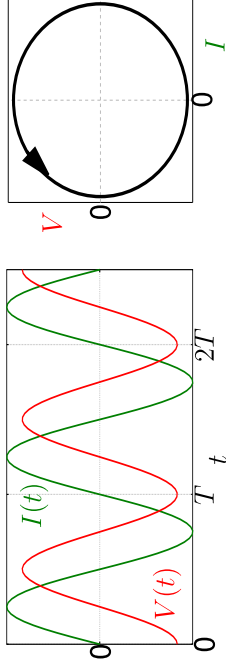
## C circuits, contd

- **Discussion: C circuits, contd**
- Current *leads* voltage by  $90^\circ$ .



## C circuits, contd

- **Definition: Capacitive reactance,  $X_C$**
- Voltage amplitude is  $V_0 = \frac{I_0}{\omega C}$ .
- Multimeter will give readings  $V_{\text{RMS}} = I_{\text{RMS}} X_C$  where


$$X_C = \frac{1}{\omega C}.$$

- $X_C$  called inductive reactance.
- **Discussion: CIVIL memory aid**
- **CIVIL** = in **C**apacitors **I** comes before **V**.
- **CIVIL** = **V** comes before **I** in inductors (**L**).



## LRC circuits [Text: Sect. 31-5]

- **Discussion: LRC circuits**

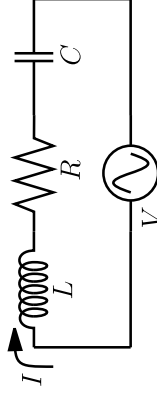

- What if circuit contains all three components in series?
- Same current  $I = I_0 \sin \omega t$  goes through each.
- Expect total voltage drop to be  $V = V_0 \sin(\omega t + \phi)$ .
- But which  $\phi$ ?  $0^\circ$ ,  $\pm 90^\circ$  or something else?
- And what is  $V_0$ ?



## LRC circuits, contd

- **Discussion: LRC circuits, contd**
- From Kirchoff's loop rule,
 
$$V = V_R + V_L + V_C$$


$$= I_0 R \sin \omega t + I_0 (X_L - X_C) \cos \omega t.$$
- **Definition: Impedance**
- After some geometry (hand waving) we find  $V_0 = I_0 Z$ .
- Likewise, multimeters will read  $V_{\text{RMS}} = I_{\text{RMS}} Z$  where

$$Z = \sqrt{R^2 + (X_L - X_C)^2}.$$


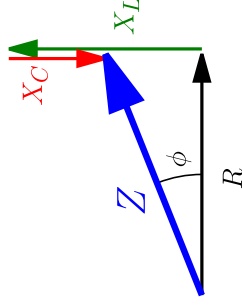
## LRC circuits, contd

- **Definition: Impedance, contd**
- $Z$  called impedance of circuit.
- “Impedes” current flow like resistance but also phase-shifts it by  $\phi$ .
- Vector representation:



## LRC circuits, contd

- **Definition: Impedance, contd**

Summary:

Name	Symbol	Phase shift
Resistance	$R$	$0^\circ$
Reactance	$X$	$\pm 90^\circ$
Impedance	$Z$	$\phi$ ( $ \phi  \leq 90^\circ$ )

- **Interactive Quiz: PRS 15b**
- **Derivation: Power**
- $L$  and  $C$  don't lose energy, they just swap it back and forth.
- Only  $R$  loses energy, as heat.



## LRC circuits, contd

- **Derivation: Power, contd**
- Average rate of power consumption is  $\bar{P} = I_{\text{RMS}}^2 R$ .
- From vector representation we see  $R = Z \cos \phi$  so

$$\bar{P} = I_{\text{RMS}}^2 Z \cos \phi = I_{\text{RMS}} V_{\text{RMS}} \cos \phi.$$

- $\cos \phi$  called **power factor**.



## Resonance [Text: Sect. 31-6]

- **Discussion: Resonance**
- Already saw a LC circuit (without any voltage source) oscillates at frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$ .
- What is so special about that frequency?
- If we “push” an LRC circuit with an AC source at frequency  $\omega_0$ ,

$$X_L = \omega_0 L = \sqrt{\frac{L}{C}},$$


$$X_C = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}}.$$

- So  $X_L = X_C$ .



## Resonance, contd

### • Discussion: Resonance, contd

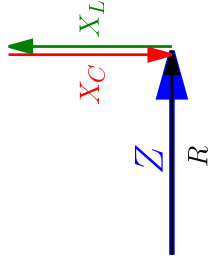

- So  $\phi = 0$  and  $Z = R$ . Changing  $\omega$  can only make  $Z$  bigger.

### • Interactive Quiz: PRS 15c



## End

### • Practice Problems:

- Ch. 31: Q. 1, 3, 5, 7, 9, 11, 13, 15.
- Ch. 31: Pr. 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31, 35, 37, 39, 41, 43, 45, 51, 53.

### • Interactive Quiz: Feedback

### • Tutorial Question: tut15

